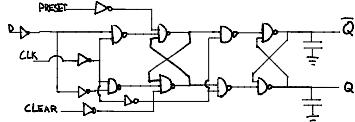


Design 1



Truth Table

PR	CLR	D	CLK	Q	Q'
0	0	X	X	1	0
1	0	X	X	0	1
0	0	X	X	X	X
1	1	0	0	0	1
1	1	0	0	0	1
1	1	1	0	0	1
1	1	1	1	1	0

Logical Effort
 $G = \prod g_i$
 $G_{NOT} = 1$
 $G_{2NAND} = 4/3$
 $G_{3NAND} = 5/3$

Calculations w/out PRESET & CLEAR
 on slave (truth table remains same)

Logical Effort

$$G = (1)(1)(1)\left(\frac{4}{3}\right)\left(\frac{4}{3}\right)\left(\frac{4}{3}\right) = \frac{256}{81}$$

Branching Effort

$$\frac{C_{in_path} + C_{out_path}}{C_{out_path}} = \left(\frac{2+4}{3}\right)\left(\frac{4+5}{4}\right)(1)(1) = \frac{62}{12}$$

Path Effort

$$F = GBH = \left(\frac{256}{81}\right)\left(\frac{62}{12}\right)\left(\frac{40}{3}\right)$$

$$= \frac{27440}{81}$$

Delay

$$D = N\hat{f} + P$$

$$D = \sqrt{\frac{27440}{81}} + 11$$

$$= 26.8$$

Electrical Effort

$$H = \frac{45+4}{3} = \frac{49}{3}$$

Parasitic Delay

$$P = 1+1+2+3+2+2 = 11$$

Best Stage Effort

$$f = \sqrt{F} = \sqrt{\frac{27440}{81}} = 2.64$$

Sizing

$$C_{in} = \frac{Count \cdot g_i}{f \cdot g_o}$$

$$C_{in_x} = \frac{45}{2.64 \cdot \frac{4}{3}} = 45A$$

$$C_{in_y} = \frac{45.9}{2.64 \cdot \frac{4}{3}} = 25.18$$

$$C_{in_z} = \frac{23.18 \cdot \frac{4}{3}}{2.64 \cdot \frac{4}{3}} = 39.69$$

$$C_{out_x} = \frac{(39.69)(\frac{4}{3})}{2.64} = 20.04$$

$$C_{out_y} = \frac{(20.04)(1)}{2.64} = 7.59$$

$$C_{out_z} = \frac{(20.04+7.59)10}{2.64} = 10.47$$

Recalculating after Sizing

Logical Effort

Does not change,
 $G = \frac{560}{81}$

$$H = \frac{45+45.9}{3} = \frac{90.9}{3}$$

Branching Effort

$$B = \frac{(C_{in_w} + C_{in_y})(C_{in_x} + C_{in_y})}{C_{in_w}} = \frac{(20.04+7.59)(39.69+23.18)}{7.59} = 9.87$$

$$P = 1+1+2+3+2+2 = 11$$

Path Effort

$$F = GBH = \left(\frac{560}{81}\right)(9.87)\left(\frac{40.9}{3}\right) = 1181.8$$

$$\hat{f} = \sqrt{1181.8} = 3.25$$

Delay

$$D = N\hat{f}'^N + P$$

$$= 6(3.25) + 11$$

$$C_{in_z} = \frac{(45)(\frac{4}{3})}{(3.25)^N} = 31.27$$

$$C_{in_y} = \frac{(31.27)(\frac{4}{3})}{(3.25)} = 12.83$$


$$C_{in_x} = \frac{(12.83)(\frac{5}{3})}{3.25 - \frac{5}{3}} = 13.49$$

$$C_{out_w} = \frac{(13.49)(\frac{4}{3})}{3.25} = 5.53$$

$$C_{out_y} = \frac{(5.53)(1)}{3.25} = 1.7$$

$$C_{out_z} = \frac{(5.53+1.7)(1)}{3.25} = 2.22$$

Design 2

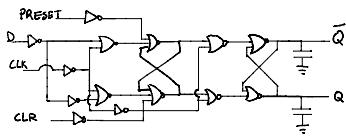

PR	CLR	D	CLK	Q	Q'
0	0	X	X	1	0
1	0	X	X	0	1
0	0	X	X	X	X
1	1	0	0	0	1
1	1	0	0	0	1
1	1	1	0	0	1
1	1	1	1	1	0

Logical Effort
 $G = (1)(1)(\frac{5}{3})(\frac{4}{3})(\frac{5}{3})(\frac{5}{3}) = \frac{875}{81}$

Electrical Effort
 $H = \frac{45+5}{3} = \frac{50}{3}$

Branching Effort
 $B = \left(\frac{31.27}{3}\right)\left(\frac{7.59}{3}\right) = \frac{32}{5}$

Parasitic Delay
 $P = 1+1+2+3+2+2 = 11$

Path Effort
 $F = GBH = \left(\frac{560}{81}\right)\left(\frac{50}{3}\right)\left(\frac{32}{5}\right) = \frac{280000}{243}$

Best Stage Effort
 $\hat{f} = \sqrt{F} = \sqrt{\frac{280000}{243}} = 3.238$

Nominu

Sizing

After Resizing

Logical Effort

Does not change
 $G = \frac{560}{81}$

$$H = \frac{45+47.73}{3} = 30.49$$

Branching Effort

$$B = \frac{(C_{in_w} + C_{in_y})(C_{in_x} + C_{in_y})}{C_{in_w}} = \frac{(32.63+10.48)(63.99+24.57)}{24.57} = 15.17$$

$$P = 1+1+2+3+2+2 = 11$$

$$B = \frac{(32.63+10.48)(63.99+24.57)}{24.57} = 15.17$$

Path Effort

$$F = GBH = \left(\frac{560}{81}\right)(15.17)(30.49) = 3241.9$$

$$\hat{f} = \sqrt{F} = \sqrt{3241.9} = 3.847$$

Delay

$$D = N\hat{f}'^N + P$$

$$= 6(3.847) + 11$$

Sizing

$$C_{in_z} = \frac{Count \cdot g_i}{f \cdot g_o}$$

$$C_{in_y} = 45 \cdot \frac{5}{3} = 24.347$$

Logical Effort

Does not change
 $G = \frac{560}{81}$

$$H = \frac{45+34.397}{3} = 26.47$$

Branching Effort

$$B = \frac{(C_{in_w} + C_{in_y})(C_{in_x} + C_{in_y})}{C_{in_w}} = \frac{(4.95+2.587)(2.297+14.9)}{2.297} = 7.389$$

$$P = 1+1+2+3+2+2 = 11$$

Path Effort

$$F = GBH = \left(\frac{560}{81}\right)(26.47)(7.389) = 1351.89$$

$$\hat{f} = \sqrt{1351.89} = 3.325$$

Delay

$$D = N\hat{f}'^N + P$$

$$= 6(3.325) + 11$$

$$C_{in_z} = \frac{45 \cdot (5/3)}{3.325} = 45.22$$

$$\frac{280000}{243} = 3.238$$

Delay

$$D = N \hat{f} + P$$

$$= 6(3.238) + 11$$

$$= 30.427$$

Sizing

$$C_{in} = \frac{C_{out} + g_i}{\hat{f} - g_o}$$

at Latches, no g_i without Latches

$$C_{in_2} = \frac{(45)(\frac{4}{3})}{\hat{f} - \frac{4}{3}} = 47.73$$

$$C_{in_y} = \frac{(47.73)(\frac{4}{3})}{\hat{f}} = 24.57$$

$$C_{in_x} = \frac{(24.57)(\frac{4}{3})}{\hat{f}} = 63.38$$

$$C_{inv} = \frac{(32.63)(\frac{4}{3})}{\hat{f}} = 32.63$$

$$C_{in_u} = \frac{(10.08 + 32.63)(\frac{4}{3})}{\hat{f}} = 13.19$$

$$D = N \hat{f} + P = 6(3.238) + 11 = 34.02$$

$$\log_{3.59}(3241.9) = 6.32$$

$$C_{in} = \frac{C_{out} + g_i}{\hat{f} - g_o}$$

at latches

$$C_{in_2} = \frac{45(\frac{4}{3})}{\hat{f} - \frac{4}{3}} = 34.347$$

$$C_{in_y} = \frac{(34.347)(\frac{4}{3})}{\hat{f}} = 14.9$$

$$C_{in_x} = \frac{(14.9)(\frac{4}{3})}{\hat{f}} = 22.97$$

$$C_{inv} = \frac{(22.97)(\frac{4}{3})}{\hat{f}} = 4.95$$

$$C_{in_u} = \frac{(4.95)(1)}{\hat{f}} = 2.587$$

$$C_{in_u} = \frac{(2.587 + 4.95)(1)}{\hat{f}} = 3.259$$

Delay

$$D = N \hat{f} + P$$

$$= 6(3.325) + 11$$

$$= 30.95$$

$$\log_{3.59}(1561.84) = 5.6$$

Sizing

$$C_{in_2} = \frac{45(\frac{4}{3})}{\hat{f} - \frac{4}{3}} = 45.22$$

$$C_{in_y} = \frac{45.22(\frac{4}{3})}{\hat{f}} = 22.66$$


$$C_{in_x} = \frac{(22.66)(\frac{4}{3})}{\hat{f}} = 53.71$$

$$C_{inv} = \frac{(53.71)(\frac{4}{3})}{\hat{f}} = 26.72$$

$$C_{in_u} = \frac{(26.72)(1)}{\hat{f}} = 8.04$$

$$C_{in_u} = \frac{(8.04 + 26.72)(1)}{\hat{f}} = 10.45$$

Design 3

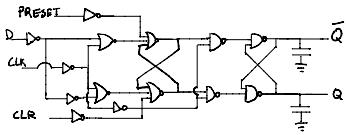

Logical Effect

$$G = (1)(1)(\frac{5}{3})(\frac{7}{3})(\frac{4}{3})(\frac{4}{3}) = \frac{560}{81}$$

Electrical Effect

$$H = \frac{45+4}{3} = \frac{49}{3}$$

Branching Effect

$$B = (\frac{3+5}{3})(\frac{7+4}{4}) = \frac{22}{3}$$

Parasitic Delay

$$P = 1+1+2+3+2+2 = 11$$

Path Effect

$$F = GBH = (\frac{560}{81})(\frac{26}{3})(\frac{4}{3}) = \frac{60560}{729}$$

Best Stage Effect

$$\hat{f} = \sqrt{N/F} = \sqrt{\frac{60560}{729}} = 3.06$$

Delay

$$D = N \hat{f} + P = (6)(2.897) + 11 = 28.38$$

Sizing

$$C_{in_2} = \frac{(45)(\frac{4}{3})}{\hat{f} - \frac{4}{3}} = 34.66$$

$$C_{in_y} = \frac{(34.66)(\frac{4}{3})}{\hat{f}} = 15.08$$

$$C_{in_x} = \frac{(15.08)(\frac{4}{3})}{\hat{f}} = 4.813$$

$$C_{inv} = \frac{(4.813)(\frac{4}{3})}{\hat{f}} = 26.18$$

$$C_{in_u} = \frac{(26.18)(1)}{\hat{f}} = 8.5$$

$$C_{in_u} = \frac{(8.5 + 26.18)(1)}{\hat{f}} = 11.53$$

Logical Effect

$$G = (1)(1)(\frac{5}{3})(\frac{7}{3})(\frac{4}{3})(\frac{4}{3}) = \frac{560}{81}$$

Electrical Effect

$$H = \frac{45+3+4}{3} = \frac{50}{3} = 26.55$$

Branching Effect

$$B = \left(\frac{C_{in} + C_{in_y}}{C_{in}} \right) \left(\frac{C_{in} + C_{in_x}}{C_{in}} \right)$$

$$B = \left(\frac{15.08 + 4.813}{15.08} \right) \left(\frac{26.18 + 8.5}{8.5} \right) = 5.338$$

Path Effect

$$F = GBH = \left(\frac{560}{81} \right) (5.338) (26.55)$$

$$= 979.9$$

Delay

$$D = N \hat{f} + P$$

$$= 6(3.15) + 11$$

$$= 29.91$$

Parasitic Delay

$$P = 1+1+2+3+2+2 = 11$$

Best Stage Effect

$$\hat{f} = \sqrt{979.9} = 3.15$$

Sizing

$$C_{in_2} = \frac{(45)(\frac{4}{3})}{\hat{f} - \frac{4}{3}} = 32.998$$

$$C_{in_y} = \frac{(32.998)(\frac{4}{3})}{\hat{f}} = 13.46$$

$$C_{in_x} = \frac{(13.46)(\frac{4}{3})}{\hat{f}} = 39.81$$

$$C_{inv} = \frac{(39.81)(\frac{4}{3})}{\hat{f}} = 21.05$$

$$C_{in_u} = \frac{(21.05)(1)}{\hat{f}} = 6.68$$

$$C_{in_u} = \frac{(6.68 + 21.05)(1)}{\hat{f}} = 8.799$$

Logical Effect

$$G = (1)(1)(\frac{5}{3})(\frac{7}{3})(\frac{4}{3})(\frac{4}{3}) = \frac{560}{81}$$

Electrical Effect

$$H = \frac{45+32.998}{3} = 26$$

Branching Effect

$$B = \left(\frac{C_{in} + C_{in_y}}{C_{in}} \right) \left(\frac{C_{in} + C_{in_x}}{C_{in}} \right)$$

$$B = \left(\frac{31.16 + 13.46}{31.16} \right) \left(\frac{21.05 + 6.68}{6.68} \right) = 8$$

Path Effect

$$F = GBH = \left(\frac{560}{81} \right) (26) (8) = 1438.558$$

Best Stage Effect

$$\hat{f} = \sqrt{1438.558} = 3.36$$

Delay

$$D = N \hat{f} + P$$

$$= 6(3.36) + 11$$

$$= 31.16$$

Sizing

$$C_{in_2} = \frac{(45)(\frac{4}{3})}{\hat{f} - \frac{4}{3}} = 29.607$$

$$C_{in_y} = \frac{(29.607)(\frac{4}{3})}{\hat{f}} = 11.75$$

$$C_{in_x} = \frac{(11.75)(\frac{4}{3})}{\hat{f}} = 26.71$$

$$C_{inv} = \frac{(26.71)(\frac{4}{3})}{\hat{f}} = 13.25$$

$$C_{in_u} = \frac{(13.25)(1)}{\hat{f}} = 3.94$$

$$C_{in_u} = \frac{(3.94 + 13.25)(1)}{\hat{f}} = 5.12$$